


# CPSC 359 Assignment 1 Report

## Summary:

This sequential circuit simultaneously controls a system including a set of Red, Yellow and Green “Car lights” and a set of Red and Green “pedestrian lights” based on the ticks 0-11 of a clock. Initially, at tick 0, the state of the lights is at state “Car Green (CG)” and “Pedestrian Red (PR)”, and then moves through a series of light combinations. After tick 11, the clock and circuit reset back to the initial state - tick 0.

---


## Final Circuit

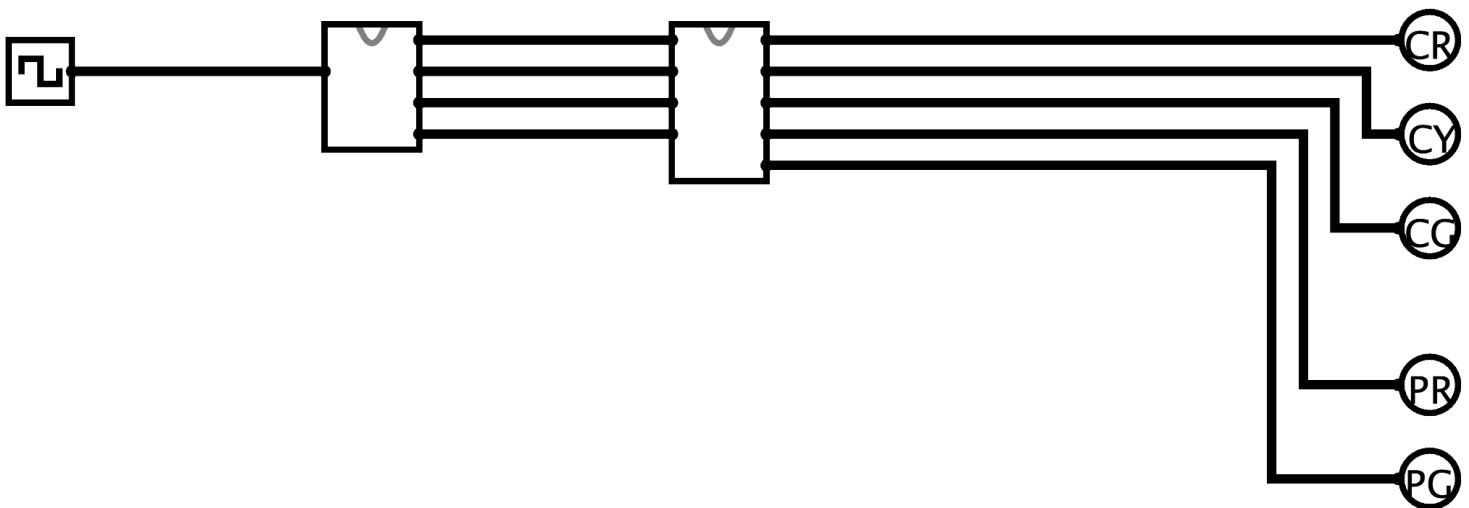

Car Green: CG  
Car Yellow: CY  
Car Red: CR  
Pedestrian Green: PG  
Pedestrian Red: PR

# Controller

Finite State Machine:

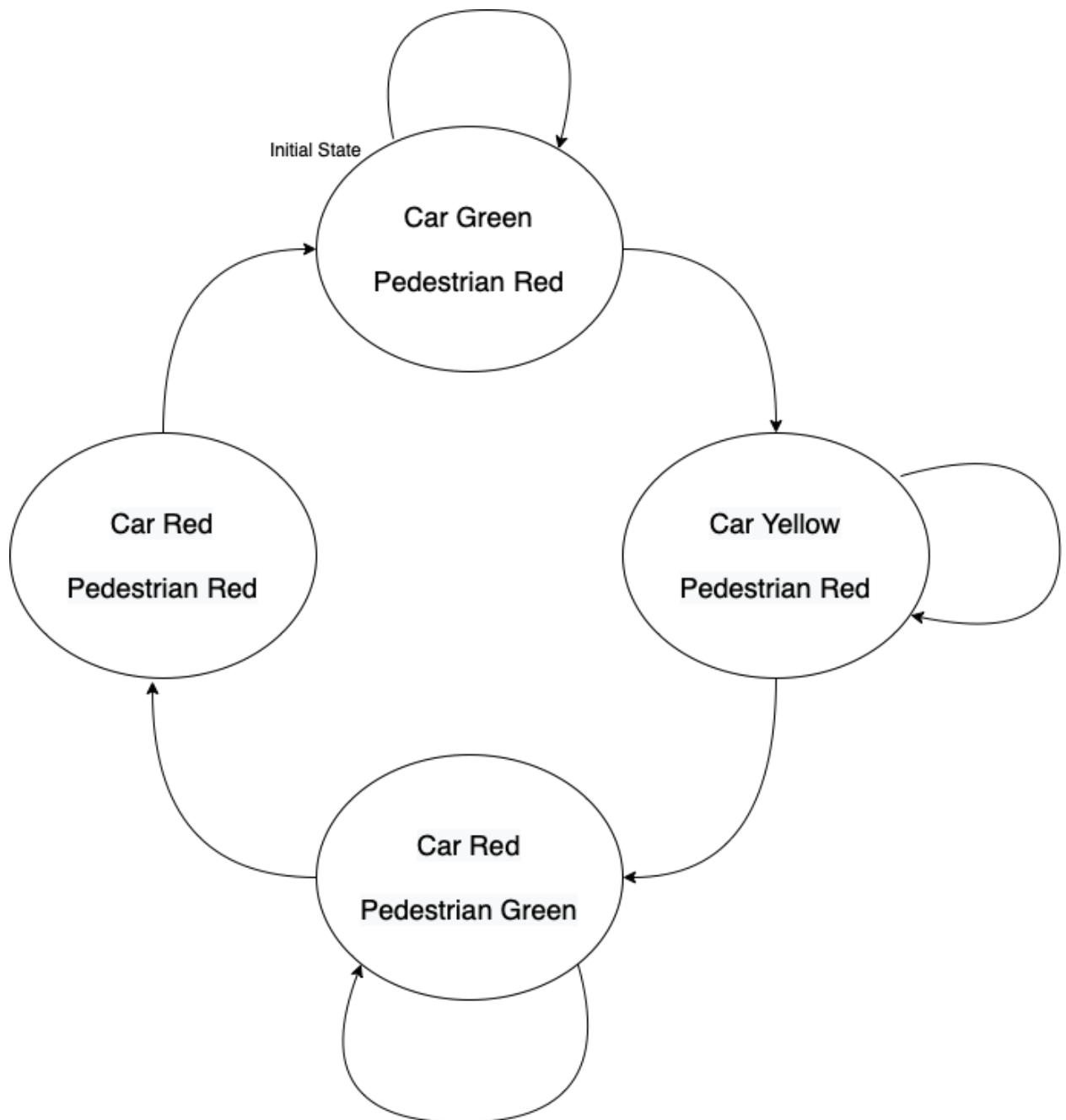

## Controller Truth Table:

no.	x	y	z	w	Car CR CY CG	Pedestrian PG PR
0	0	0	0	0	0 0 1	0 1
1	0	0	0	1	0 0 1	0 1
2	0	0	1	0	0 0 1	0 1
3	0	0	1	1	0 0 1	0 1
4	0	1	0	0	0 0 1	0 1
5	0	1	0	1	0 0 1	0 1
6	0	1	1	0	0 1 0	0 1
7	0	1	1	1	0 1 0	0 1
8	1	0	0	0	1 0 0	1 0
9	1	0	0	1	1 0 0	1 0
10	1	0	1	0	1 0 0	1 0
11	1	0	1	1	1 0 0	0 1

Car Green: 001

Car Yellow: 010

Car Red: 100

Pedestrian Green: 10

Pedestrian Red: 01

## Controller Boolean Sum of Products & Simplification

### Car:

#### For Car Red (CR):

CR is positive at ticks 8, 9, 10 and 11 therefore the Boolean Sum of Products is:

$$= xy'z'w' + xy'z'w + xy'zw' + xy'zw$$

Simplification with K-Map

m0	m1	m3	m2
m4	m5	m7	m6
m12	m13	m15	m14
<b>m8</b>	<b>m9</b>	<b>m11</b>	<b>m10</b>

Using adjacency of m8,m9,m11,m10:

$$= xy'z'(w'+w) + xy'z(w'+w)$$

$$= xy'z' + xy'z$$

$$= xy'(z'+z)$$

$$\mathbf{CR = xy'}$$

#### For Car Yellow (CY):

CY is positive at ticks 6 and 7. Therefore the Boolean Sum of Products is:

$$= x'yzw' + x'yzw$$

Simplification with K-Map

m0	m1	m3	m2
m4	m5	<b>m7</b>	<b>m6</b>
m12	m13	m15	m14
m8	m9	m11	m10

Using adjacency of m7,m6:

$$= x'yz(w'+w)$$

$$\mathbf{CY = x'yz}$$

### For Car Green (CG):

CG is positive at ticks 0, 1, 2, 3, 4, 5. Therefore the Boolean Sum of Products is:  
$$= x'y'z'w' + x'y'z'w + x'y'zw' + x'y'zw + x'yz'w' + x'yz'w$$

Simplification with K-Map

m0	m1	m3	m2
m4	m5	m7	m6
m12	m13	m15	m14
m8	m9	m11	m10

Using adjacency of m0,m1,m3,m2 and m4,m5, m0, m1:

$$= x'y'(z'w' + z'w + zw' + zw) + x'z'(yw' + yw + y'w' + y'w)$$

$$\mathbf{CG = x'y' + x'z'}$$

---

## **Pedestrian:**

### For Pedestrian Green (PG):

PG is positive at ticks 8, 9, and 10. Therefore the Boolean Sum of Products is:  
$$= xy'z'w' + xy'z'w + xy'zw'$$

Simplification with K-Map

m0	m1	m3	m2
m4	m5	m7	m6
m12	m13	m15	m14
m8	m9	m11	m10

Using adjacency of m8,m9 and m8, m10:

$$= xy'z'w' + xy'z'w + xy'zw' + xy'z'w'$$

$$= xy'z'(w' + w) + xy'w'(z' + z)$$

$$\mathbf{PG = xy'z' + xy'w'}$$

**For Pedestrian Red (PR):**

PR is positive at ticks 0, 1, 2, 3, 4, 5, 6, 7, 11. Therefore the Boolean Sum of Products is:

$$= x'y'z'w' + x'y'z'w + x'y'zw' + x'y'zw + x'yz'w' + x'yz'w + x'yzw' + x'yzw + xy'zw$$

Simplification with K-Map

m0	m1	m3	m2
m4	m5	m7	m6
m12	m13	m15	m14
m8	m9	m11	m10


Using adjacency of m0,m1,m3,m2 and m4,m5, m7, m6 and m3, m11:

$$= x'y'(z'w' + z'w + zw' + zw) + x'y(z'w' + z'w + zw' + zw) + xy'zw + x'y'zw$$

$$= x'y' + x'y + y'zw$$


$$\mathbf{PR = x' + y'zw}$$

## Controller Combinational Circuit:

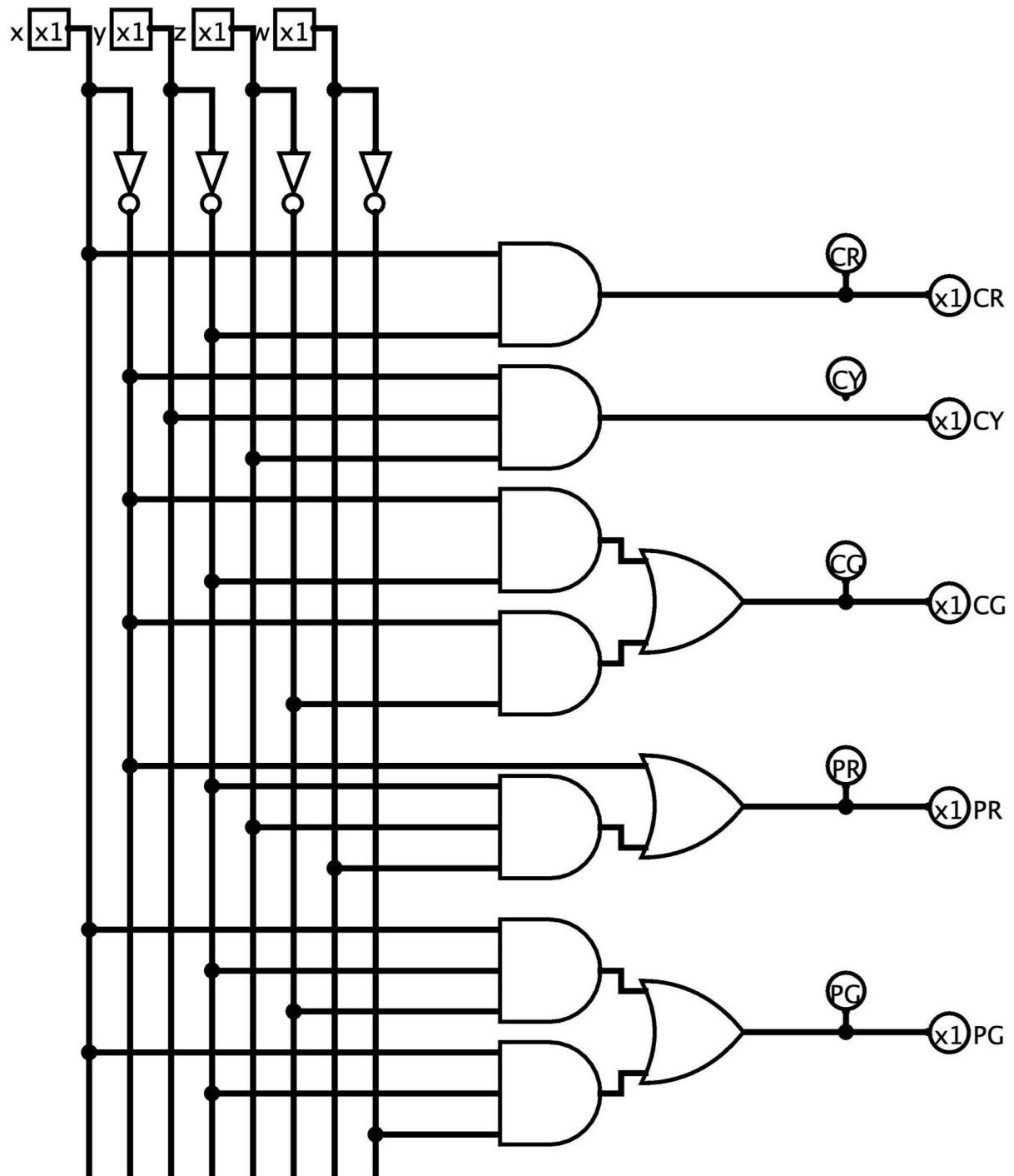

# Counter

Finite State Machine:

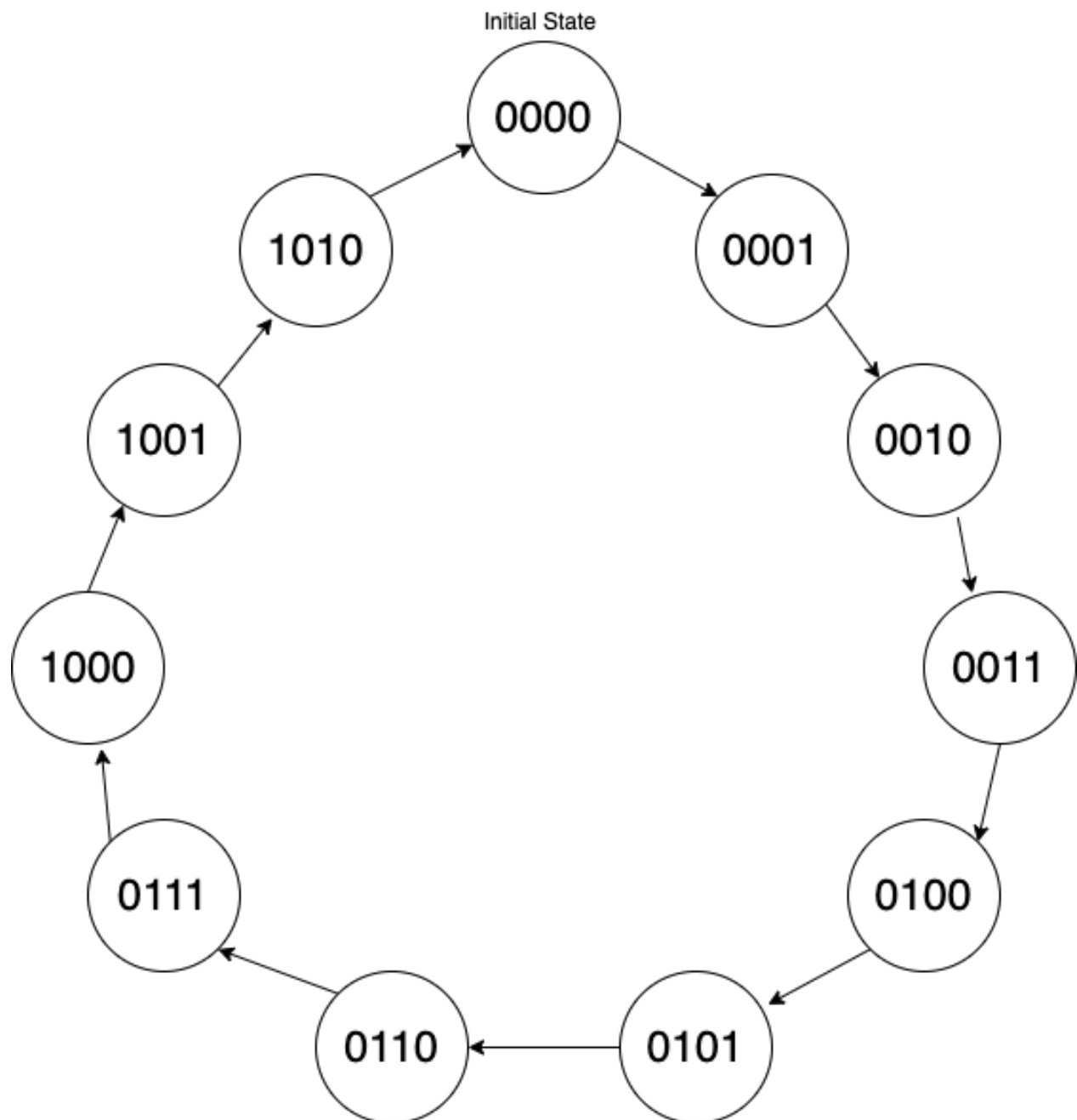



## Counter Truth Table:

x	y	z	w	Jx	Kx	Jy	Ky	Jz	Kz	Jw	Kw
0	0	0	0	0	X	0	X	0	X	1	X
0	0	0	1	0	X	0	X	1	X	X	1
0	0	1	0	0	X	0	X	X	0	1	X
0	0	1	1	0	X	1	X	X	1	X	1
0	1	0	0	0	X	X	0	0	X	1	X
0	1	0	1	0	X	X	0	1	X	X	1
0	1	1	0	0	X	X	0	X	0	1	X
0	1	1	1	1	X	X	1	X	1	X	1
1	0	0	0	X	0	0	X	0	X	1	X
1	0	0	1	X	0	0	X	1	X	X	1
1	0	1	0	X	0	0	X	X	0	1	X
1	0	1	1	X	1	0	x	X	1	X	1

## Controller Boolean Sum of Products & Simplification

Jx:  $x'yzw$

Kx:  $xy'zw$

Jy:  $x'y'zw$

Ky:  $x'yzw$

**Jz:** w

**Kz:** w

**Jw:**  $x'y'z'w' + x'y'zw' + x'yz'w' + x'yzw' + xy'z'w' + xy'zw'$

m0	m1	m3	m2
m4	m5	m7	m6
m12	m13	m15	m14
m8	m9	m11	m10

**Jw after simplification:**  $y'w' + x'w'$

**Kw:** 1

## Counter Sequential Circuit:

